

DC electricity 直流电

• def. (current & voltage)

• 电: 运输能量/信息

• charge (Q): physical property of matter that causes it to experience a force when placed in an electromagnetic field.

单位: coulomb (C) $Q = \text{电子数} \times 1.6 \times 10^{-19}$


• current (A): the rate of flow of charge $I = \frac{\Delta Q}{\Delta t}$ $\Delta Q = I \Delta t$

是 scalar 但有方向, 流向与正电荷相同. 负电荷相反

• potential: energy carried on per unit charge 电流从势差高 \rightarrow 低

• potential difference (V): energy transferred from each unit
 $\frac{J}{C}$ $V = \frac{W}{Q}$ ← work done by charge

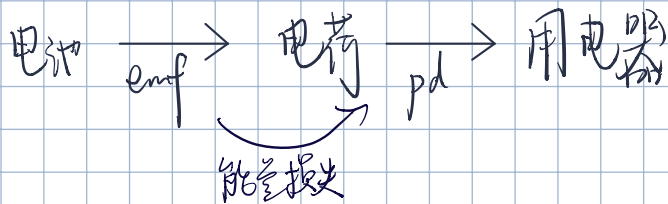• electromagnetic force: energy transferred to each unit 电流从势差高到低



- 命题术语: ① current through ...
② voltage across ...
③ emf of ...

• def. (power & efficiency)

power (W): rate of energy transfer

$$P = \frac{W}{t} = \frac{W}{Q} \times \frac{Q}{t} = IV$$

$$\text{efficiency} = \frac{E_{in}}{E_{out}}$$

• 电子在迁移过程中的能量变化

金属内的 free e: $hf_{thres} = \phi + \frac{1}{2}mv^2$

半导体内的价带 e: $eV_{thres} = hf + \frac{1}{2}mv^2$

气体原子内的 e: $hf(eV) = \Delta E_n$

● Resistance


def: $R = \frac{V}{I}$ unit: ohm (Ω)

↳ 大小由材料内能决定, 内能大, 扰动剧烈, 电子被干扰大, R大



$P = IV = I^2R = \frac{V^2}{R}$

欧姆定律:


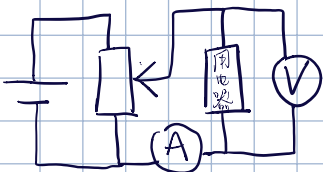
the current through a component is directly proportional to the voltage across it.





温度恒定的电阻

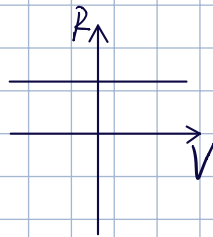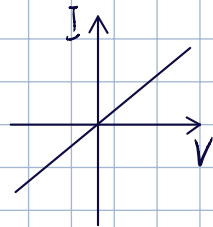



ptc
灯泡 filament
(T↑R↑)

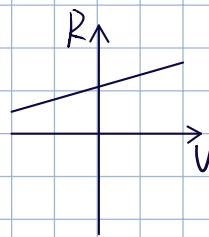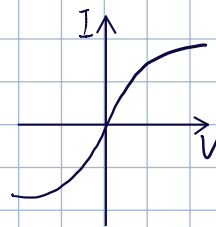

ntc
热敏电阻
(T↑R↓)

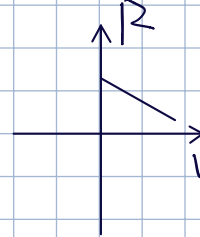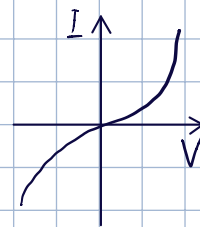

二极管
(单向流通)

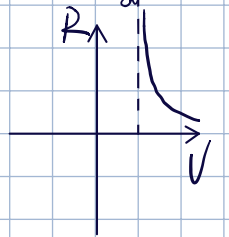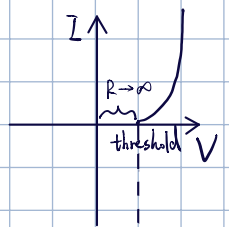


一些容易短路:

$I \uparrow \rightarrow E \uparrow (e^- \rightarrow \text{lattice}) \rightarrow \text{lattice vibration} \uparrow \rightarrow f \text{ of collision} \uparrow \rightarrow v \downarrow \xrightarrow{I = nqAv} I \downarrow \rightarrow R \uparrow$

热敏: $V \uparrow \rightarrow E \uparrow \rightarrow N_{\text{free}} \uparrow \xrightarrow{I = nqVA} I \uparrow \xrightarrow{R = \frac{V}{I}} R \downarrow \rightarrow \Delta I \uparrow$
(穿过晶格的电子数量)


● Resistivity (ρ): $R = \frac{\rho l}{A}$ 横截面积 unit: Ωm

由材料和温度决定

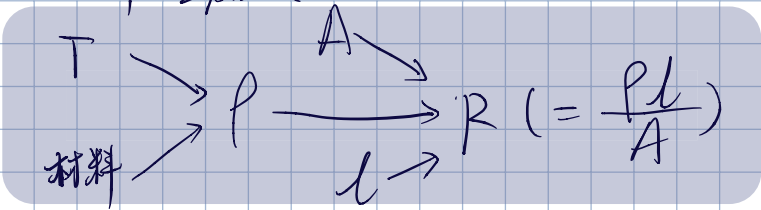

Condition of different material.

● transport equation

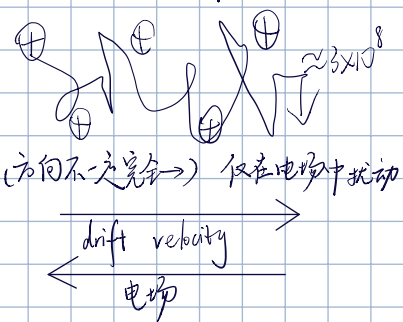

影响因素 $\left\{ \begin{array}{l} \text{emf} \uparrow \rightarrow V \uparrow \\ T \uparrow \rightarrow V \uparrow \end{array} \right.$

def. drift velocity: the average overall speed of the electrons in material (受电场操控)



电流公式 $\left\{ \begin{array}{l} \text{定义式: } I = \frac{\Delta Q}{\Delta t} \text{ (定义)} \\ I = \frac{V}{R} \\ I = nqVA \end{array} \right.$

n → charge carrier density m^{-3}
 v → drift velocity
 A → 1.6×10^{-19}



● Conductions in metal & semiconductor

分类标准 ↓

三者本质区别: 导带和价带间的距离

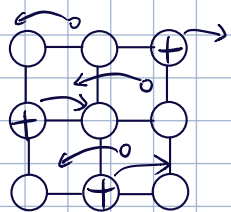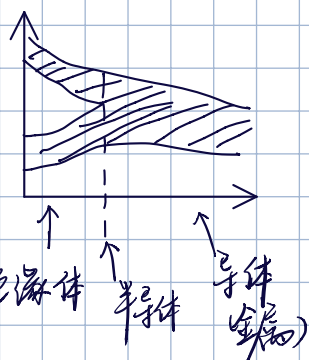

电场中电子与离子反向跑。
 绝缘体: 电子离子不动
 导体: 电子离子乱跑

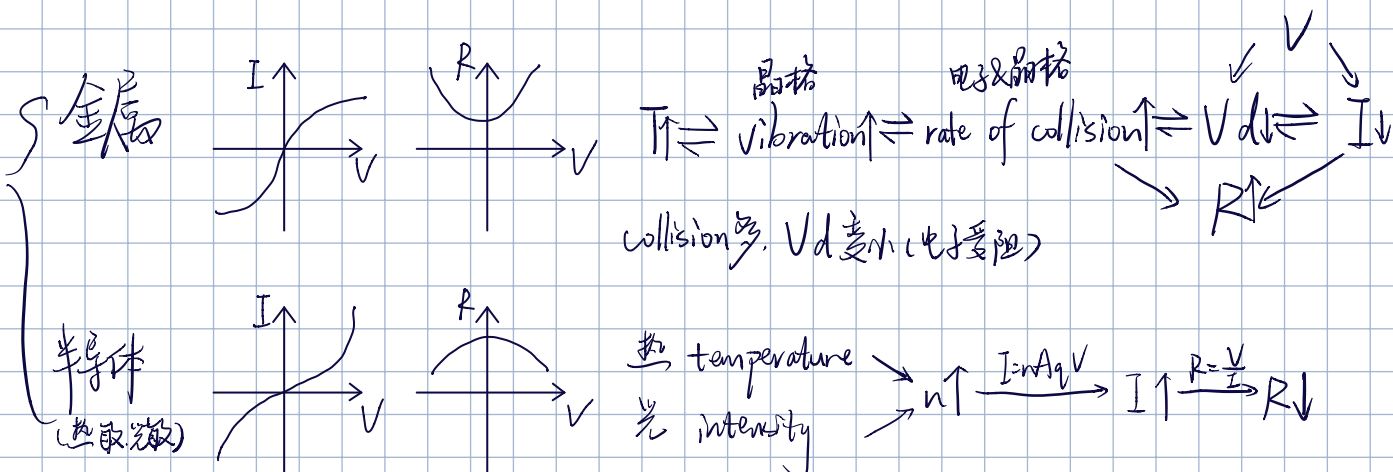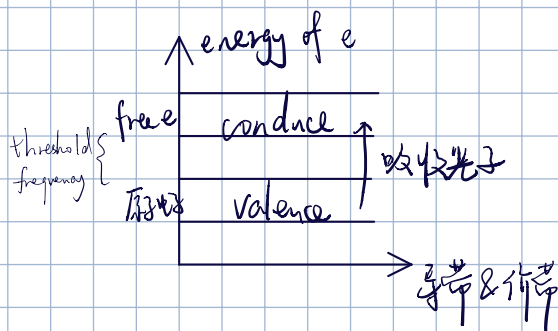


求电阻直接用 $\frac{V}{I}$, 不可求解, 电阻是状态量


串联 & 并联

一些类比

Parallel circuit

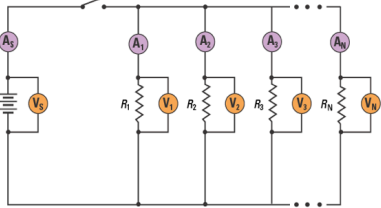

Series circuit

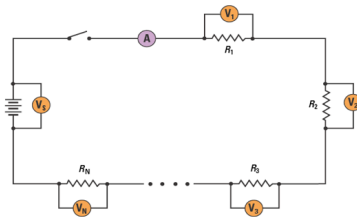

λ - electron
 mass - charge
 $\Delta GPE - \Delta EPE$
 $\Delta GPE - p.d.$
 $\Delta EPE - emf.$

并联
 In parallel

$$\begin{cases} I_s = I_1 + I_2 + \dots \\ V_s = V_1 = V_2 = \dots \\ \frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots \end{cases}$$

解释题
 $R_{total} < R_n$
 $R_n \uparrow \quad R_{total} \uparrow$

串联
 In series

$$\begin{cases} I_s = I_1 = I_2 = \dots \\ V_s = V_1 + V_2 + \dots \\ \frac{V_1}{R_1} = \frac{V_2}{R_2} = \dots \end{cases}$$

Kirchhoff's Rules

First rule: current rule \rightarrow 遵守 charge conservation


At any junction point, the sum of all currents entering the junction must equal to the sum of all currents leaving the junction.

Second rule: voltage rule \rightarrow 遵守 Δ potential conservation

In closed loop, changes in potential must be 0
 \rightarrow 包括电源


计算步骤

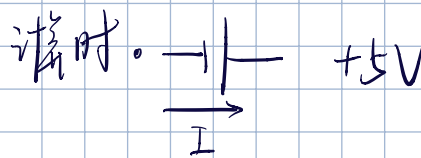- ① 假设电流方向
- ② $k > 2$ 找 $(n-1)$ 个 loop 关系式
- ③ k_1 补齐式子
- ④ 求解



其它用 $\sum \frac{emf}{R} - IR$


分压电路

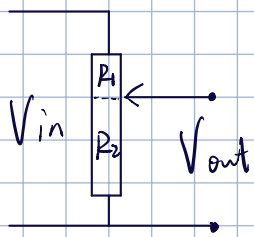

$$V_{out} = V_{in} \times \frac{R_2}{R_1 + R_2}$$

论述: the ratio of potential difference is the ratio of resistance

解释 (电表对电路的干扰)

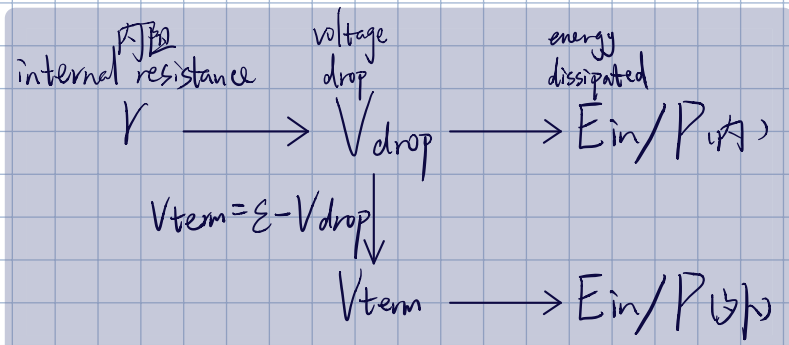

$$\begin{aligned} \mathcal{E} &= I_V + I R \\ \downarrow & \quad \downarrow \quad \uparrow \\ \text{emf of cell} & \quad \text{voltage drop (内阻电压)} \quad \text{terminal voltage} \end{aligned}$$

$$\Sigma I = I_V^2 + I^2 R$$

① R_A 小 $R_A \approx 0$ 串联 $\rightarrow R_{\text{总不变}} \rightarrow I$ 不变

② R_V 大 $R_V \approx \infty$ 并联 $\rightarrow R_{\text{parallel}} \approx R \rightarrow V$ 不变

③ R_V 大 $R_V \approx \infty$ 测内阻 $\rightarrow V \approx \mathcal{E}$

④ R_V 大 R_A 大 $R_V \approx \infty$ 并联 $\rightarrow I_V \approx 0$ $I_A = I_V + I_R \rightarrow I_A \approx I_R$
 R_A 大 串联 $\rightarrow V_A$ 大 V_V 不影响

⑤ R_A 小 R_V 无影响 $R_A \approx 0$ 串联 $\rightarrow V_A \approx 0$ $V_V = V_R + V_A \rightarrow V_{\text{总}} \approx V_R$
 R_V 小 并联 $\rightarrow I_V$ 大 I_A 不影响

⑥ $R_V \approx \infty$ 并联 $\rightarrow I_V \approx 0$ $I_A = I_{\text{总}} - I_V \rightarrow I_A \approx I_{\text{总}}$

实验

{ process
accuracy

1. object \rightarrow equation

2. measurements

{ variable
constants

{ independant 自变量
dependant 因变量

3. apparatus

4. measure & average (少见)

4. measure y for various x

5. plot y-x graph

6. determine gradient

7. 测得的量 = 斜率

	x	y	a	b	...
1					
2					
3					
...					

● 测电阻率

$$\rho = \frac{RA}{L}$$

2. inde var: l de var: I constant: V. diameter

3. ruler. A-meter. micrometer. V-meter

4. x-y $\frac{1}{I} - L$

5. gradient linear point = $\frac{1}{IL} = \frac{\rho}{VA}$

$$\rho = \frac{VA}{IL}$$

● 误差

① measure

length

{ 夹子: use clip with small size (夹子下方长度要在阻值内)
铁丝拉直 (strengthen the wire)
尺子: 金属条 // 尺子. parallel error.

diameter

{ not uniform 多测取平均
(micrometer) zero error

resistivity

{ contact: resistance of circuit wire
small R for V-meter
zero error

Ⓐ 会比实际大, 因为 Ⓥ 有电阻.
选阻值尽量大的电压表

② 误差

③ error

{ systematic: 校 0. 热差. contact R
random: repeat & average